

# AND GATE

- A logic gate is a physical device that implements a Boolean function
- It performs a logical operation on one or more logic inputs and produces a single logic output.
- AND gate takes two inputs and gives output as low(0) whenever any of its input is low(0).
- The representation of **AND** function is  **$C=A.B$**

# AND GATE

- It performs a logical operation on one or more logic inputs and produces a single logic output.
- AND gate takes two inputs and gives output as low(0) whenever any of its input is low(0).
- The representation of **AND** function is  $C=A.B$

[  
label=AND] Truth Table for AND gate

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1



Figure: AND gate

# OR GATE

- OR gate takes two inputs and gives output as high(1) whenever any of its input is high(1), else it gives low(0).
- It is represented as  $C=A+B$

# OR GATE

- OR gate takes two inputs and gives output as high(1) whenever any of it's input is high(1),else it gives low(0).
- It is represented as  $C=A+B$

Truth Table for OR gate

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1



Figure: OR gate

# NOT GATE

- NOT gate is different from previous two in the sense that it has 1 input instead of two.
- The output is high(1) if input is low(0) and vice versa.

# NOT GATE

- NOT gate is different from previous two in the sense that it has 1 input instead of two.
- The output is high(1) if input is low(0) and vice versa.

Truth Table for NOT gate

A	B
0	1
1	0



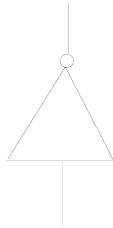


Figure: NOT gate

# De-Morgan's Laws

The rules given by De-Morgan allow the expression of conjunctions and disjunctions purely in terms of each other via negation. Refer to slides 1, 3, and 5 before going further.

# De-Morgan's Laws

The rules given by De-Morgan allow the expression of conjunctions and disjunctions purely in terms of each other via negation. Refer to slides 1, 3, and 5 before going further.

## Laws

The laws if laid in plain English are as follows:

- 1 The negation of a conjunction is the disjunction of the negations.
- 2 The negation of a disjunction is the conjunction of the negations.

## Theorem

*The negation of a conjunction is the disjunction of the negations.  
Represented mathematically:*

$$\overline{A + B} = \overline{A}.\overline{B} \quad (1)$$

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

### Proof using Truth Table

A	B	A+B	A'	B'	(A+B)'	A'.B'
0	0	0	1	1	1	1
0	1	1	1	0	0	0
1	0	1	0	1	0	0
1	1	1	0	0	0	0

## Theorem

*The negation of a disjunction is the conjunction of the negations.  
Represented mathematically:*

$$\overline{A.B} = \overline{A} + \overline{B} \quad (2)$$

$$\overline{A.B} = \overline{A} + \overline{B}$$

### Proof using Truth Table

A	B	AB	A'	B'	AB'	A'+B'
0	0	0	1	1	1	1
1	0	0	0	1	1	1
0	1	0	1	0	1	1
1	1	1	0	0	0	0

# Generalised De-Morgan's Laws

The law can be extended to more than two inputs following the definition itself.



# Generalised De-Morgan's Laws

The law can be extended to more than two inputs following the definition itself.

## Laws

$$\overline{(A + B + C + D + E.....)} = \overline{A}.\overline{B}.\overline{C}.\overline{D}.\overline{E}..... \quad (3)$$

$$\overline{(A.B.C.D.E.....)} = \overline{A} + \overline{B} + \overline{C} + \overline{D} + \overline{E}..... \quad (4)$$